

Simulation results can be seen on the figure below.

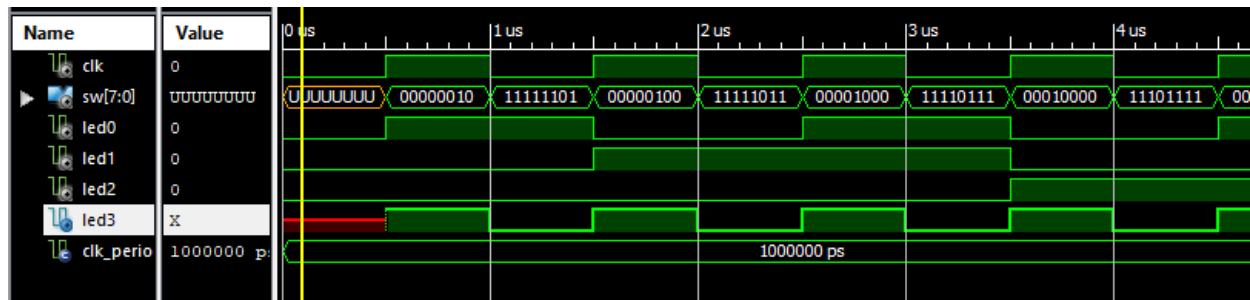


Figure 11. – Simulation of multiplexer circuit

Finally implement the circuit and analyze its operation.